



# Welcome to The Logic Design Lab!

## Fall 2022 Lab 1: Gate-Level Verilog

Prof. Chun-Yi Lee

Department of Computer Science  
National Tsing Hua University

# Agenda

- Lab 1 Outline
- Lab 1 Basic Questions
- Lab 1 Advanced Questions
- Basic Concept of Verilog Testbench



# Lab 1 Outline

- Basic questions (1.5%)
  - Individual assignment
  - Due on **9/22/2022. In class.**
  - Only demonstration is necessary. Nothing to submit.
- Advanced questions (5%)
  - Group assignment
  - eeclass submission due on **9/29/2022. 23:59:59.**
  - Demonstration on your FPGA board (**In class**)
  - Assignment submission (**Submit to eeclass**)
    - Source codes and testbenches
    - Lab report in PDF

# Lab 1 Rules

- Only gate-level description is permitted
  - Only basic logic gates are ALLOWED (AND, OR, NAND, NOR, NOT)
  - Sorry, no XOR & XNOR
- Please AVOID using
  - Continuous assignment and conditional operators
  - Behavioral operators (e.g., =, +, -, &, |, ^, &&, !, ~....., etc.)

# Lab 1 Submission Requirements

- Source codes and test benches
  - Please follow the templates **EXACTLY**
  - We will test your codes by TAs' testbenches
- Lab 1 report
  - Please submit your report in a single **PDF** file
  - Please **draw** the gate-level circuits of your designs
    - Remember **not to draw them by hands**
  - Please **explain** your designs in detail
  - Please **list** the contributions of each team member clearly
  - **Please explain how you test your design**
  - What you have **learned** from Lab 1

# Agenda

- Lab 1 Outline
- **Lab 1 Basic Questions**
- Lab 1 Advanced Questions
- Basic Concept of Verilog Testbench




# Basic Questions

- Individual assignment
- Verilog questions (due on **9/22/2022. In class.**)
  - (Gate-level) 4-bit 4-to-1 multiplexer (abbreviated as MUX)
  - (Gate-level) 1-bit D flip-flop (DFF) with D Latches
- Please demonstrate your work by **waveforms**
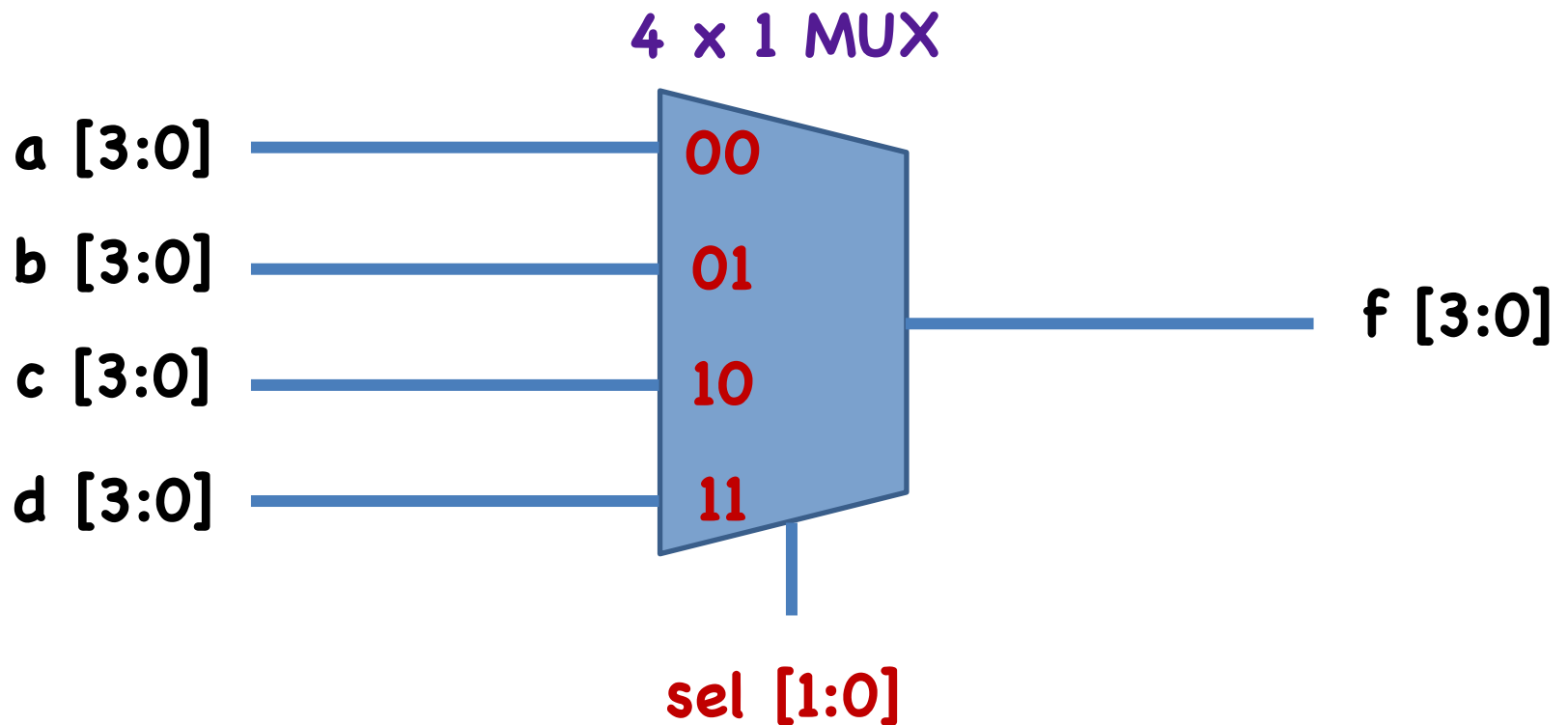
# Verilog Basic Question 1


- (Gate-level) 4-bit 4-to-1 multiplexer (MUX)
- Construct your 4-to-1 MUX with three 2-to-1 MUXes





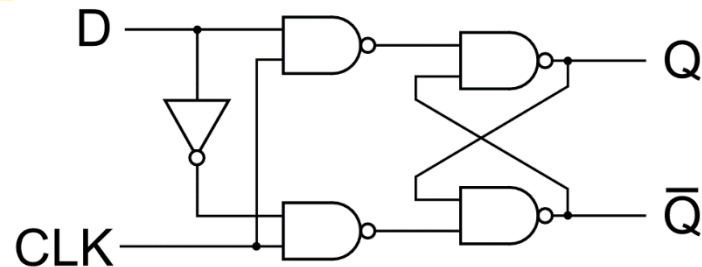
# Verilog Basic Question 2

- (Gate Level) 1-bit D Flip-Flop (DFF) with D Latches
- Design a **latch** module as follows:



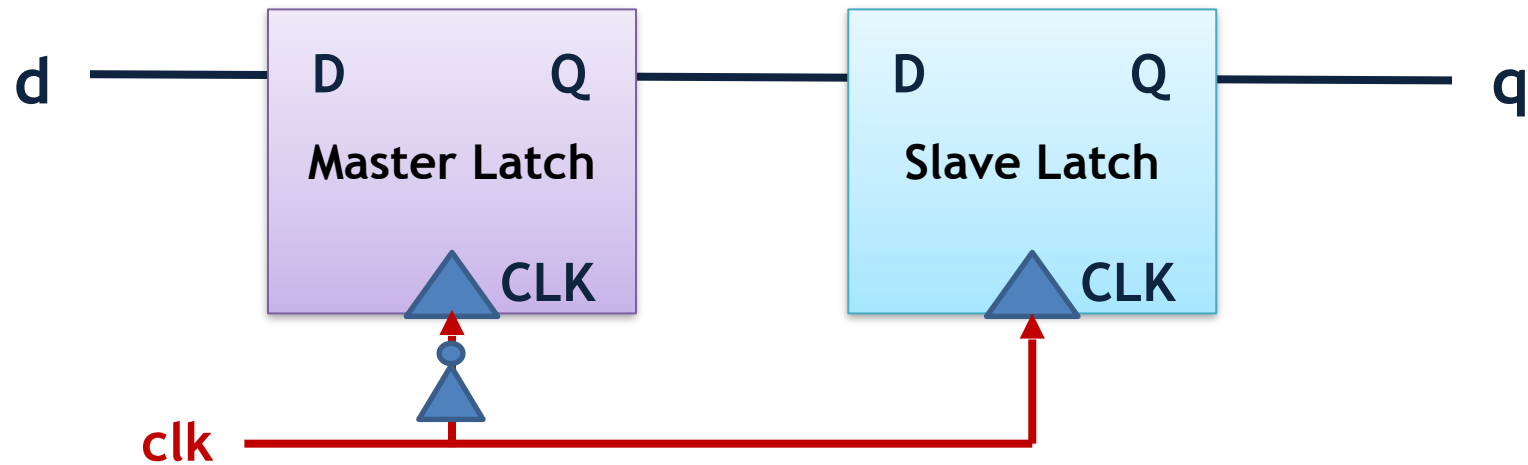- Then design a **clk positive** edge trigger **flip-flop** module as:



- We will test your **latch** and **flip-flop** by TA's testbenches

# Agenda

- Lab 1 Outline
- Lab 1 Basic Questions
- **Lab 1 Advanced Questions**
- Basic Concept of Verilog Testbench




# Advanced Questions

- Group assignment
- Verilog questions (due on 9/29/2022. 23:59:59.)
  - (Gate-level) 4-bit 1-to-4 de-multiplexer (DMUX)
  - (Gate-level) 4-bit simple crossbar switch with MUX/DMUX
  - (Gate-level) 4-bit 4x4crossbar with simple crossbar switch
  - (Gate-level) 1-bit toggle flip flop (TFF)
- FPGA demonstration (due on 9/29/2022. In class.)
  - (Gate-level) 4-bit simple crossbar switch with MUX/DMUX

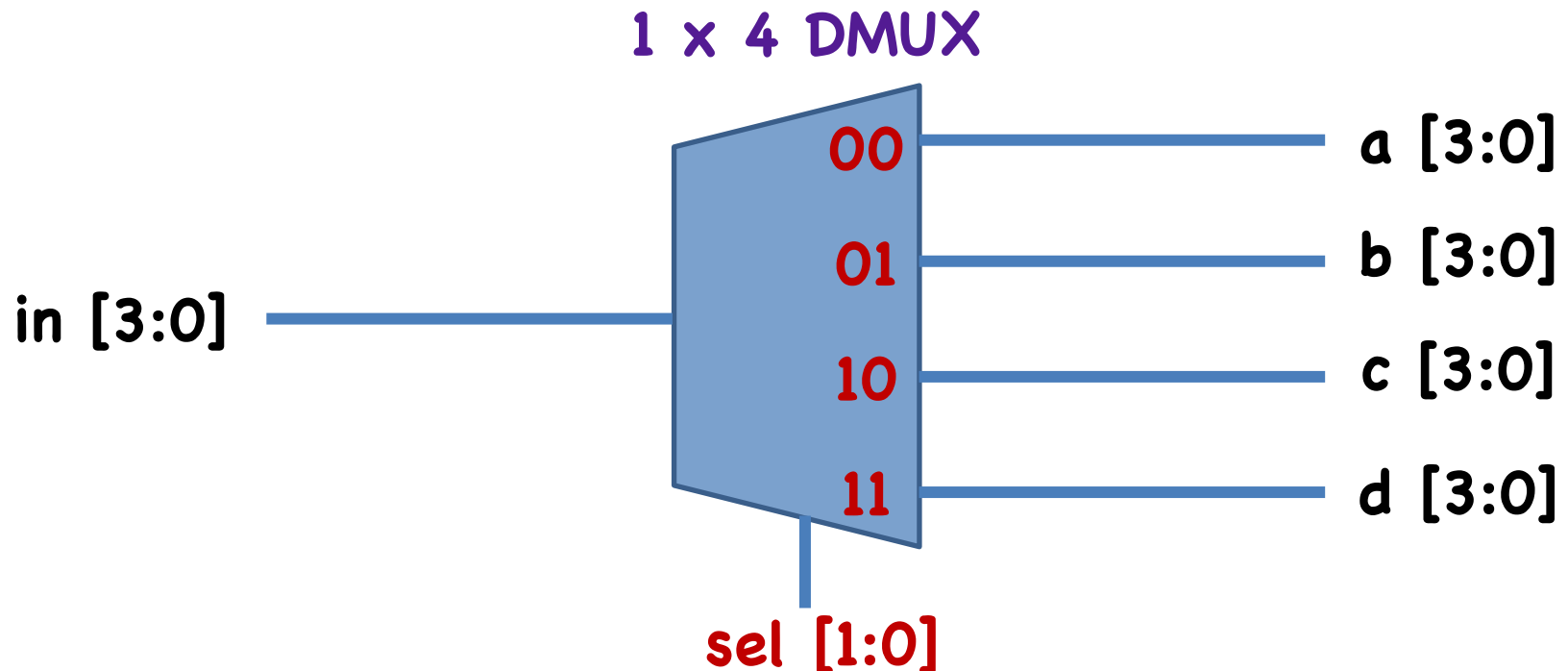
# Verilog Advanced Question 1

- (Gate-level) 4-bit 1-to-4 de-multiplexer (DMUX)
- The value of the selected output is set to **in**, while the others' are set to **0**.
- Construct your 1-to-4 DMUX with three 1-to-2 DMUXes



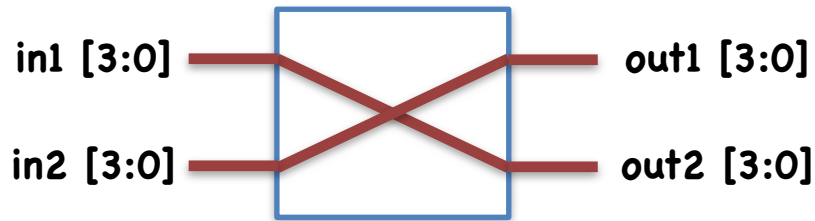
# Verilog Advanced Question 2


- (Gate-level) 4-bit simple crossbar switch with MUX/DMUX
- Reuse your 2-to-1 MUX and 1-to-2 DMUX modules



■ **control** = 1'b1

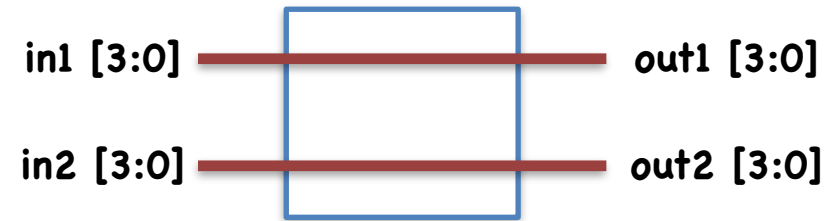


■ **control** = 1'b0

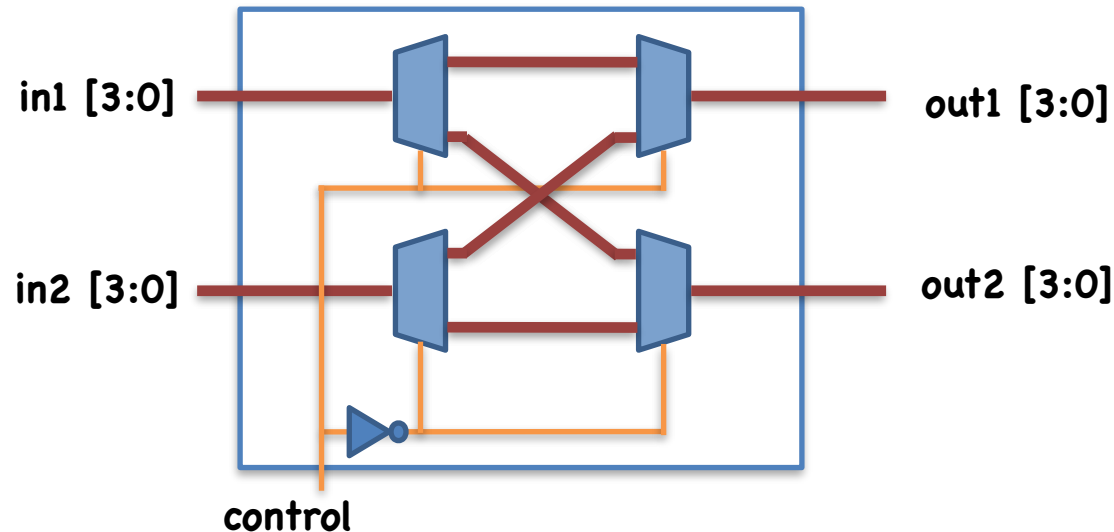

 
# Verilog Advanced Question 3

- (Gate-level) 4-bit 4x4crossbar with simple crossbar switch
- Please reuse your module in the previous question
- Some combinations of input and output pairs cannot be achieved by such a crossbar (e.g., [(in1, out3), (in2, out4), (in3, out1), (in4, out2)]). Please list all of them in your report.


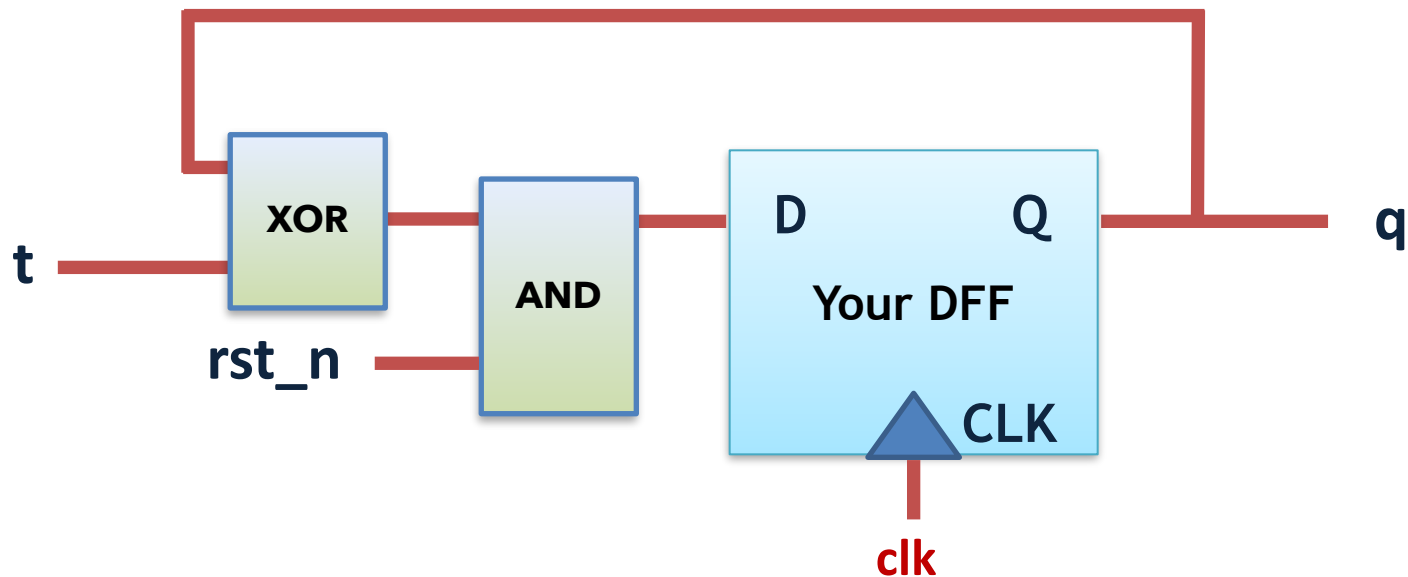
# Verilog Advanced Question 4

- (Gate-level) 1-bit toggle flip flop (TFF)
- Please reuse your design of DFF, and avoid using XOR directly




# Advanced Questions

- Group assignment
- Verilog questions (due on **9/29/2022. 23:59:59.**)
  - (Gate-level) 4-bit 1-to-4 de-multiplexer (DMUX)
  - (Gate-level) 4-bit simple crossbar switch with MUX/DMUX
  - (Gate-level) 4-bit 4x4crossbar with simple crossbar switch
  - (Gate-level) 1-bit toggle flip flop (TFF)
- **FPGA demonstration** (due on **9/29/2022. In class**)
  - (Gate-level) 4-bit simple crossbar switch with MUX/DMUX


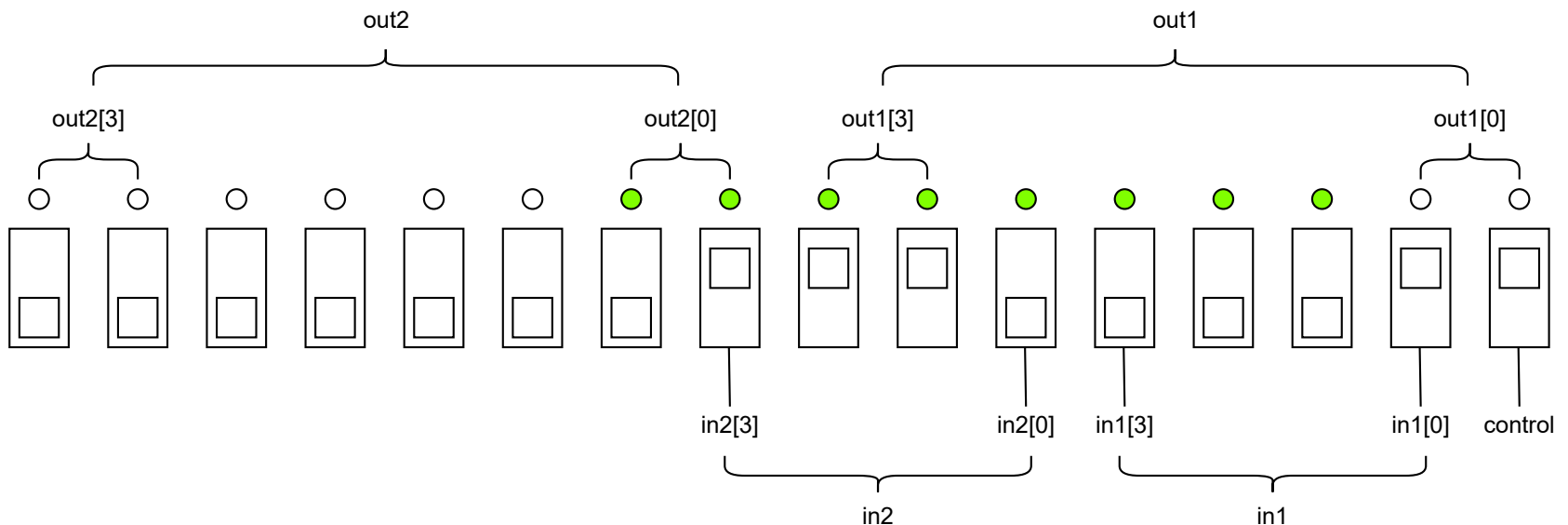
# FPGA Demonstration 1

- (Gate-level) 4-bit simple crossbar switch with MUX/DMUX
  - Please implement your gate-level 4-bit simple crossbar switch with MUX/DMUX on your FPGA board
  - Please use **SWITCHes** as your **inputs**, and **LEDs** as your **outputs**
  - Please assign your inputs/outputs as:
    - in2, in1, control: The rightmost nine **SWITCHes** , respectively
    - out2, out1: **16 LEDs (note that each output corresponds to TWO LEDs)**
    - The detailed FPGA configuration is illustrated below.




# Agenda

- Lab 1 Outline
- Lab 1 Basic Questions
- Lab 1 Advanced Questions
- **Basic Concept of Verilog Testbench**


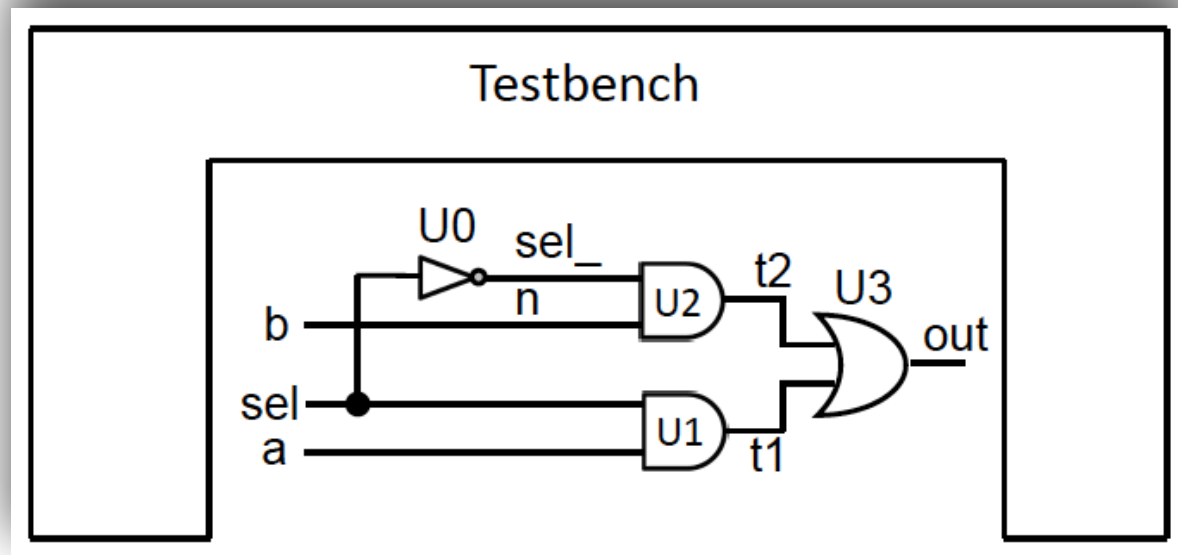
# Verilog Simulation Framework

- Testbench verifies whether a module is correct or not
- Similar to the main function in C++
- Generate stimulus and check the outputs




# Verilog Testbench

## Design

```

module Nand_Latch_1 (q, qbar, preset, clear);
  output    q, qbar;
  input     preset, clear;

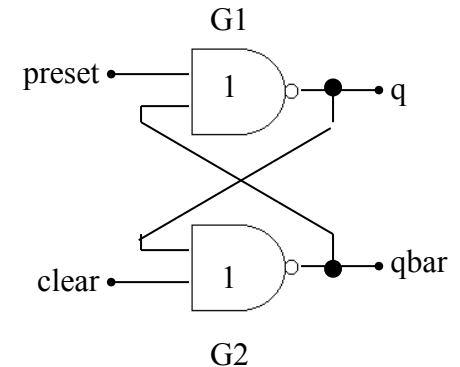  nand #1 G1 (q, preset, qbar),
        G2 (qbar, clear, q);
endmodule
  
```



## Testbench

```

`timescale 1ns / 1ps
module    test_Nand_Latch_1;
  reg     preset, clear;
  wire    q, qbar;

  Nand_Latch_1 M1 (q, qbar, preset, clear);

  always begin
    #20 clear = !clear;
  end

  initial
  begin
    preset = 1'b0; clear = 1'b1;

    #10
    preset = 1'b1;
  end
endmodule
  
```

**// Simulation Unit / Accuracy**  
**// Testbench module**  
**// Inputs should be declared as reg**  
**// Outputs should be declared as wire**

**// Instantiate YOUR DESIGN module**

**// always condition: The description always happens**  
**// The value of clear inverts every 20 ns**

**// Initial conditions**

**// Units of “Simulation Units”. In this case, 10ns**





# Thank you for your attention!

\*Seattle night view taken at LA County Museum of Arts, Los Angeles, CA.  
This picture is taken by Chun-Yi Lee himself, who is also a fan of photography